

Homework 13

Nodal analysis problems.

1. Complete the problems of the previous homework.
2. In the circuits below find current I shown in red:

